 



# Week 2 Tutorial - Building an ALU
 
## 1 Introduction

- This week, we are going to build an Arithmetic Logic Unit from scratch, using a handful of simple logic gates and other components.
- The ALU will take in two 32-bit values, and 2 control lines. Depending on the value of the control lines, the output will be the addition, subtraction, bitwise AND or bitwise OR of the inputs.
- Schematically, here is what we want to build:




- Note! This is an *interface* for the ALU: what goes in, what comes out. It also shows the ALU as an *abstraction*: you can't see how it works, but you do know what it does.
- Also note that there are three status outputs as well as the main result: is the result zero, was there a carry, and did the operation result in an overflow?
- Note: just a reminder on the difference between a carry and an overflow:
  - **Carry**: was there a carry in the most-significant bit which we could not output in the given number of bits (32 bits, above).
  - **Overflow**: does the sign of the output differ from the inputs, indicating (for example) that a sum of two positive numbers has overflowed and is now a negative result!
- Some of the data and control lines are shown with a slash and a number like 32.




- This indicates that the line is actually 32 lines in parallel, e.g. the result is 32-bits wide. If you don't see a slash in the diagrams below, you can assume that the line is only 1-bit wide.
 
### 1.1 Basic Components

- We are going to use four logic gates: AND, OR, NOT and XOR. You should have seen these already in other subjects. Below are the icons for each, and their truth table.



a	b	out
0	0	0
0	1	0
1	0	0
1	1	1

 

a	b	out
0	0	0
0	1	1
1	0	1
1	1	1




a	b	out
0	0	0
0	1	1
1	0	1
1	1	0



in	out
0	1
1	0

 - We are going to use another component, the *multiplexor*. The job of the multiplexor is to choose one of several inputs, based on a control line, and send the chosen input to the output.




## Multiplexor

- This multiplexor above is a 1-bit wide 2-way multiplexor: 2 inputs, 1 bit wide each. If you add extra control lines, you can choose more inputs: 2 control lines is used in a 4-way multiplexor, 3 control lines in an 8-way multiplexor etc.
- And by using multiple multiplexors in parallel, you can make N-bit wide multiplexors.
- I'm not going to show you the internals of the multiplexor. You should, however, know that it can be easily built with the 4 logic gates above.
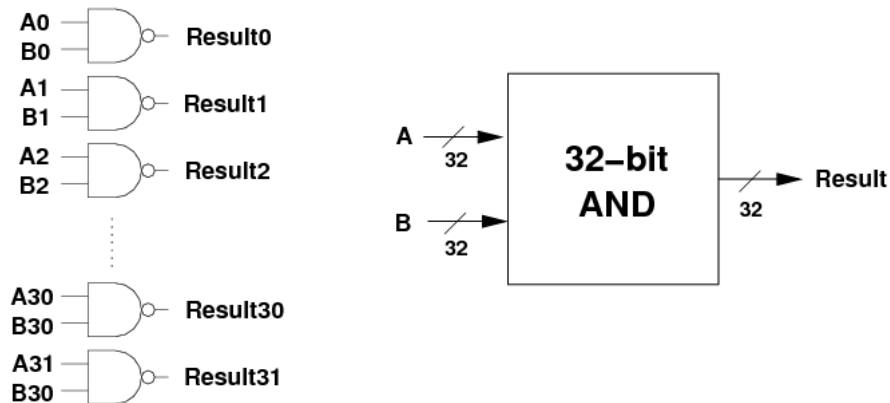
### 1.2 Bitwise AND


- Bitwise AND is very useful, for example to calculate an IP network's identity:
  - 131.245.7.18 AND 255.255.255.0  $\Rightarrow$  131.245.7.0
- Building the logic to do 32-bit AND on two inputs is easy: as each bit is independent, we just need 32 AND gates in parallel.



- Note the interface diagram on the right. Each time we build a larger component, we are going to hide it behind an interface.

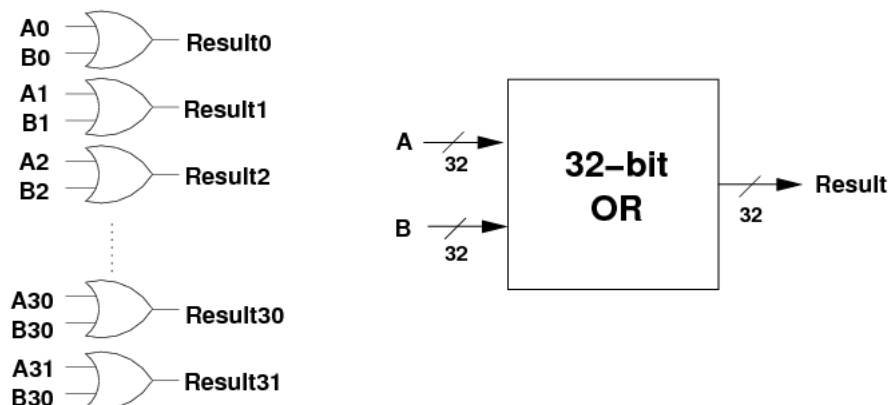
### 1.3 Bitwise OR

- 32-bit bitwise OR is just as easy as bitwise AND, we just need 32 OR gates in parallel.



 
### 1.4 Addition

- Addition isn't going to be so easy.
- We saw previously that we have to add bits, and this may produce a carry. Columns further up need to accept a carry as input, along with two inputs, and produce the 1-bit output and another carry for the next column up.
- The component which will perform a 1-bit ADD, receiving a carry in and producing a 1-bit output and a carry out is called a **full adder**. Its interface looks like the following:



 
- Internally, here is what a full adder looks like, just 5 logic gates.



- The truth table for the full adder is:

Cin	A	B	Result	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- At some point sit down, try some inputs, and convince yourself that the logic works as advertised!
- To make a 32-bit full adder, we simply have to string 32 of these 1-bit full adders together.
- Except for the least-significant adder, each one is going to receive its carry from the one below and pass up its own carry to the one above.
- For the most significant bit, if the carry is a 1, then we ran out of bits to store the result.

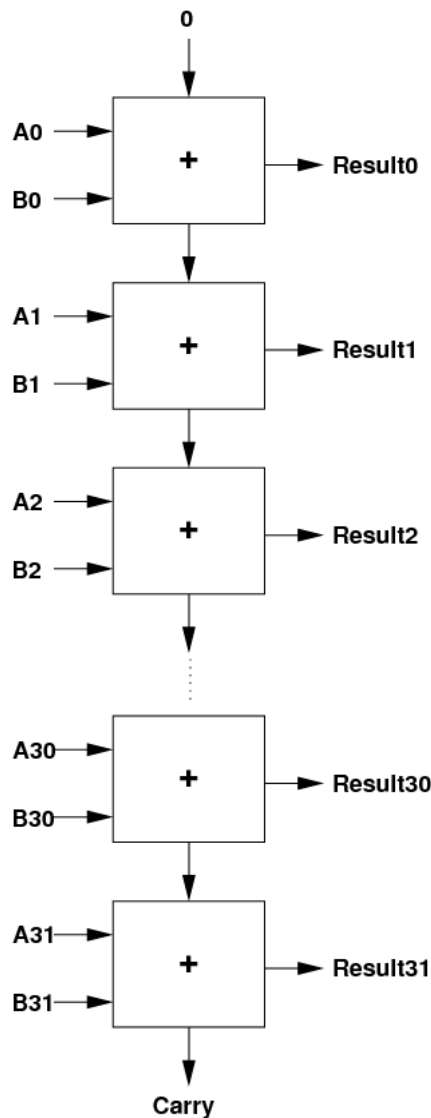


- When the final carry output is 1, this indicates that the result was too big to fit into 32 bits.
- I'm going to delay showing you the interface diagram for the 32-bit full adder, because we can modify it to also do subtraction.

### 1.5 Subtraction


- We could build a completely separate component, a 32-bit subtractor, once we work out how to build a 1-bit subtractor.
- Fortunately, we can simplify things a bit.
- According to the rules of maths:  $3-2=3+(-2)$ .
- If we could negate one of the inputs, we could use the existing 32-bit full adder.
- We have already seen two algorithms to negate a twos complement binary integer.
- One of them works as follows: invert every bit in the number, then add 1.
- Putting all of the above together, we can say:

$$A - B = A + (-B) = A + \sim B + 1$$

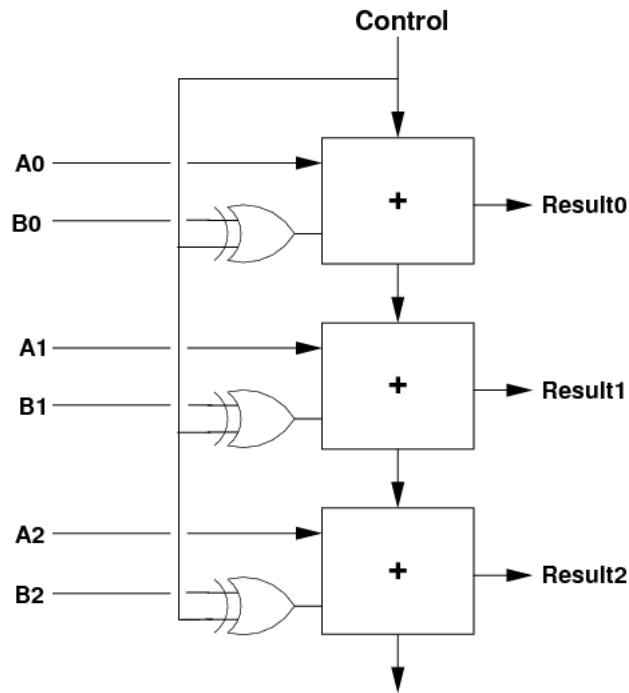- Inverting every bit is easy: we can use a NOT gate for each bit in B.
- But now we need to do  $A + \sim B + 1$ . How can we do this?
- We are going to use a very clever trick.
  - Set the initial carry-in to 1 instead of 0, thus adding an extra 1 to the sum.
  - And instead of using NOT gates, we will use XOR gates.




- If we are doing addition (Control=0), then one arm of the XOR gates is zero, and the B bits go into the adders unchanged, and the carry-in is zero.
- If we are doing subtraction (Control=1), then one arm of the XOR gates is one. This inverts all of the B bits before they get to the adders. As well, the carry-in is now 1, so we achieve the result of doing  $A - B = A + \sim B + 1$ !
- Overall, we end up with this unit which can do addition and subtraction:

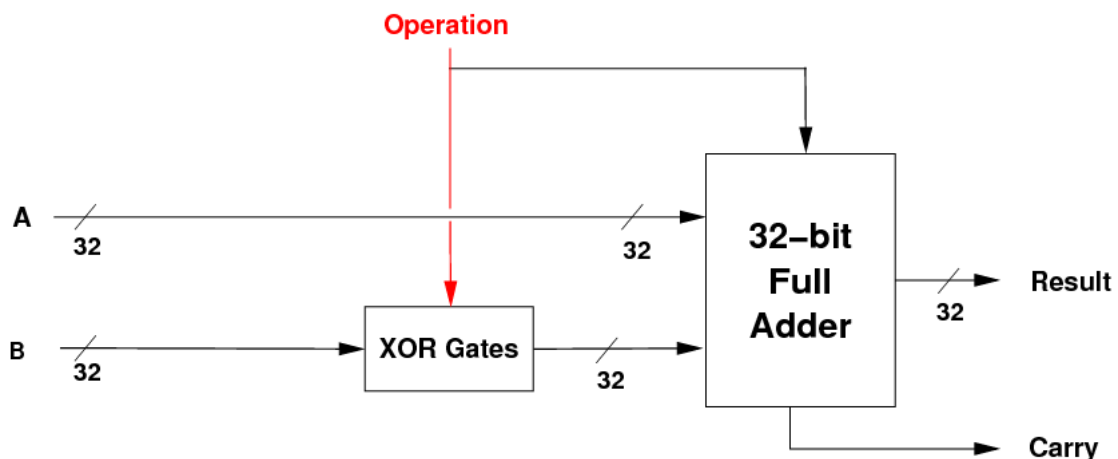

- If the operation bit is 0, we pass in B and perform  $A+B$ . If the operation bit is 1, we invert B and do  $A + \sim B + 1$ .
- We can now distinguish between **data lines** (which pass data around) and **control lines** (which control the actions of the components).
- The data lines are also known as **datapaths**.
- The *Operation* line above is a control line, as it controls the action being performed. But note, it is also used as a 1-value for the carry-in, so it is also a piece of data!
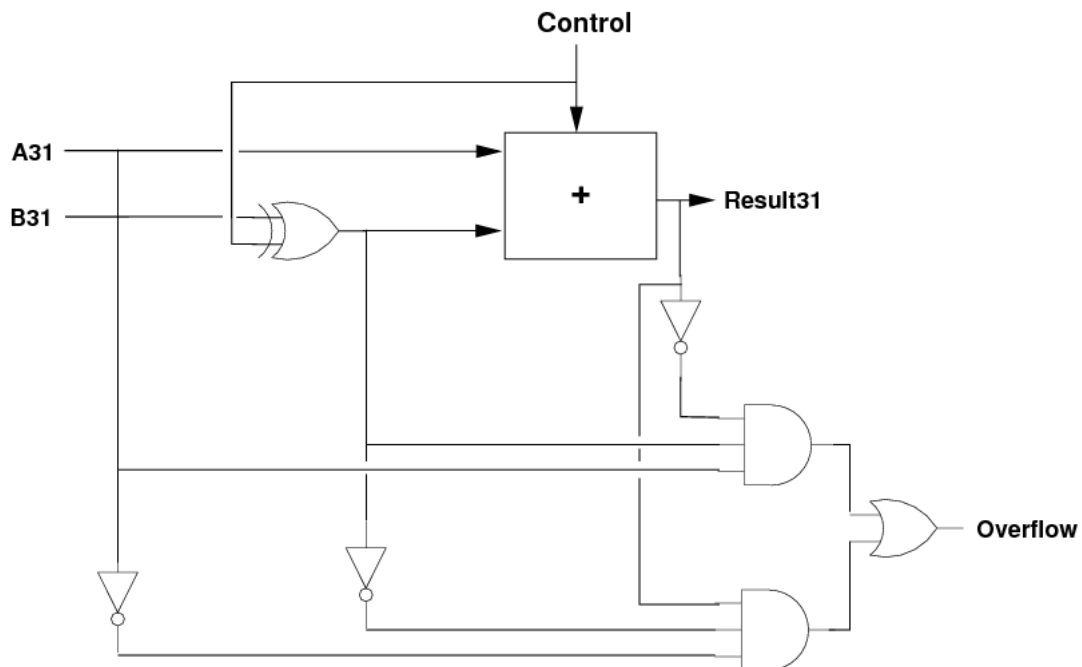
## 1.6 Overflow Output

- We've seen that a carry occurs when the final addition or subtraction is too big to fit into 32 bits.
- A related mathematical output is *overflow*. This indicates that the sign of the maths result differs from the sign of the two inputs.
- Imagine we were using 4-bit numbers: you do  $7 + 7$  and get the result -2!
- Why? Because  $7 (0111) + 7 (0111) = 1110$ , which in 4-bit two's-complement is -2.
- Overflow occurs when the size of the inputs is such that there is a carry which changes the most-significant sign bit.
- The ALU will always output both carry and overflow, but both only makes sense when the operation is add or subtract.
- When we are doing the logical operations (AND and OR), the values on the carry and overflow outputs have no meaning.
- As overflow is only maths related, this should be implemented in the ADD/SUBTRACT unit.
- The logic is follows: when adding, if the sign of the two inputs is the same, but the result sign is different, then we have an overflow.
- The boolean expression is  $[\bar{a}_{31}] \cdot [\bar{b}_{31}] \cdot \text{result}_{31} + a_{31} \cdot b_{31} \cdot [\bar{\text{result}}_{31}]$ .
- We have to do this only for addition, so we take the b31 value after the XOR gate, i.e. just as it goes into the most-significant adder.



### 1.7 Negative Output

- When is the result negative? When its most-significant bit is 1.
- We can wire this bit directly out of the ALU, so that it indicates if the result is negative.

### 1.8 Zero Output


- One thing left to do is to provide the zero output: is the result zero?
- This is only true if **all** of the bits of the result are zero. We can do this for the logical and the maths units.
- To do this, we can use a 32-bit OR gate followed by a 1-bit NOT gate:



- The OR gate outputs a 0 only if all input bits are 0. If any input bit is a 1, the OR's output is a 1.
- The NOT gate simply inverts this, giving the result:
  - if any result bit is on, the output is 0, i.e. not zero.
  - if all result bits are off, the output is 1, i.e. zero.
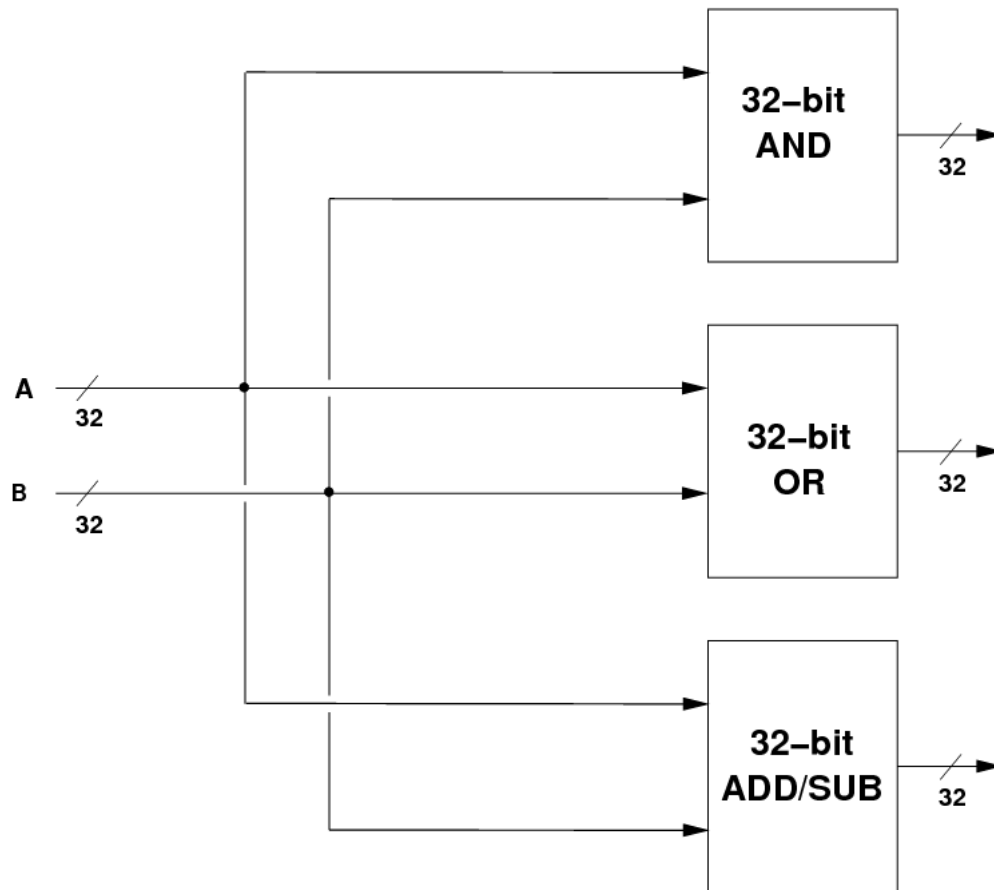
### 1.9 Putting It All Together


- We are getting close to being able to build the full ALU.
- We now have three main units:
  - a 32-bit bitwise AND unit,
  - a 32-bit bitwise OR unit, and
  - a 32-bit ADD/SUBTRACT unit with a control line.
- the logic to output carry, overflow, zero and negative.
- We can pass the inputs A and B to all three units, and perform all three operations in parallel:



- But, we need to choose which of the three results we want, based on the two control lines coming into the ALU. We would like:

$c_1$	$c_0$	Result
0	0	A AND B
0	1	A OR B
1	0	A + B
1	1	A - B

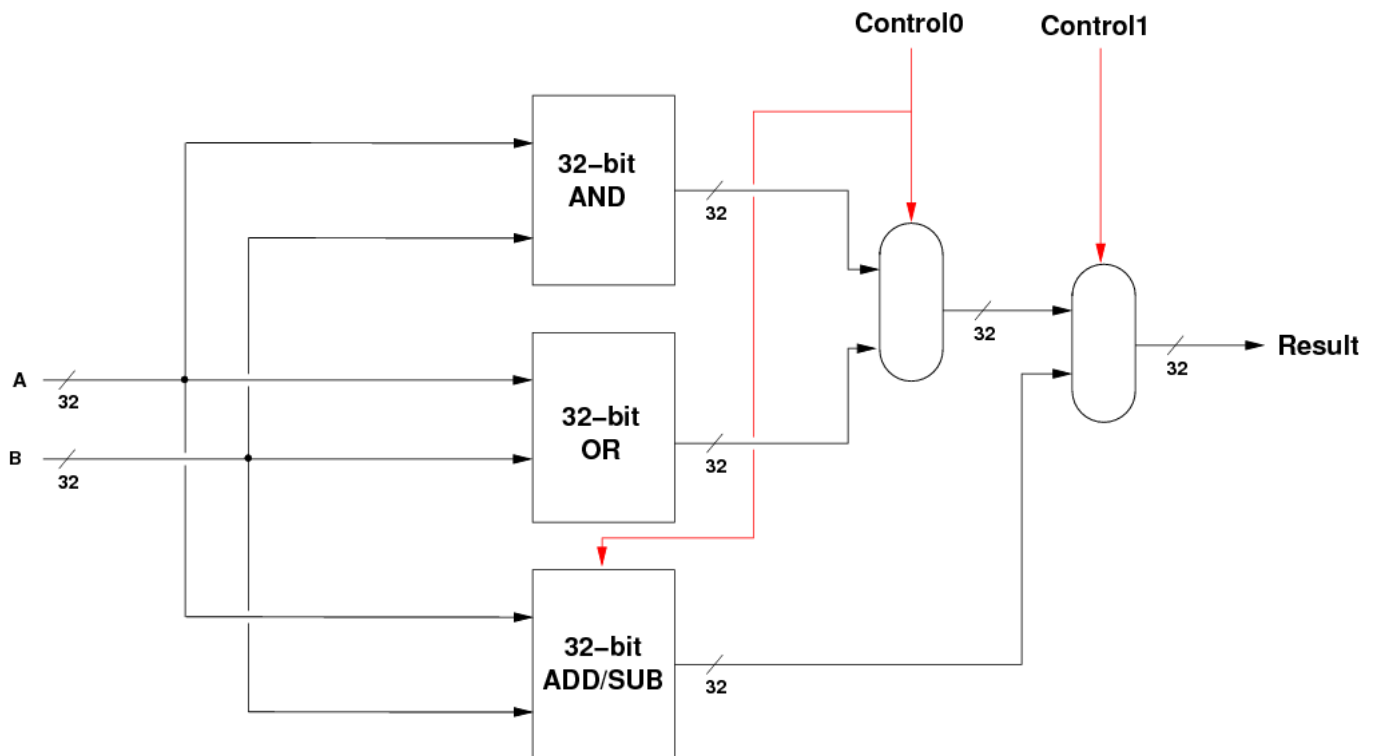
- How do we control which of the four operations actually becomes the result? With multiplexors again.



- When  $c_0=0$ , the ANDORresult is A AND B, and the ADDSUBResult is A + B.
- When  $c_0=1$ , the ANDORresult is A OR B, and the ADDSUBResult is A - B.
- Now we just have to choose between these two results, and that is done with the second multiplexor, which chooses either the bitwise logic result or the maths result.
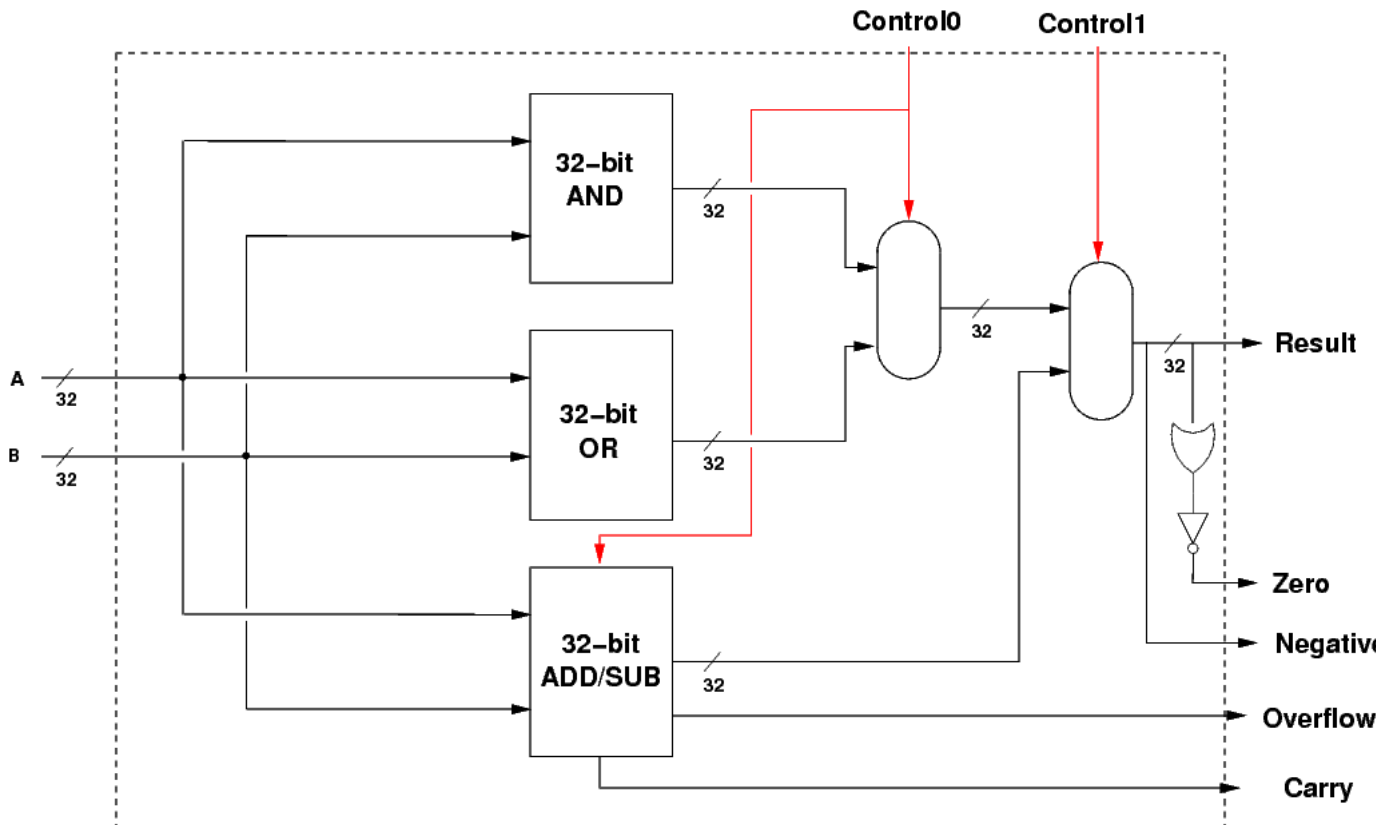
### 1.10 Finally

- To finish off, we can draw the three components, the multiplexors and the zero logic, to reveal the final 32-bit ALU.



- The dotted line shows the interface to the ALU.

### 1.11 Implementing the ALU

- Here is the above ALU implemented in Logisim: [ALUweek2.circ](#)
- This is only an 8-bit version, but extending it to be a 32-bit CPU is simple but tedious.
- Download the file, run Logisim, and open the above circuit.
- Select the Hand icon in the top-left of the Logisim window, then click on the data inputs and the two control inputs to change their values.
- Try out some additions, a subtraction, some ANDs and ORs, and satisfy yourself that the ALU works as advertised.
- See if you can put in some input values which cause an overflow.

### 1.12 Conclusion

- That's about all we can cover in terms of ALU design in this subject.
- Obviously, real ALUs perform many more operations, and use many performance optimisations.
- This is just a taste of ALU design, but you should now understand that:
  - an ALU is just a collection of logic components;
  - the logic components can be made from ordinary logic gates;
  - data can flow in parallel to multiple units;
  - everything operates in parallel: several units can produce output internally;
  - control logic, via multiplexors, chooses which output to use as the result.
- For more interested students, the ALU chapter in Patterson & Hennessy goes into much more detail and covers more operations such as multiplication and division.